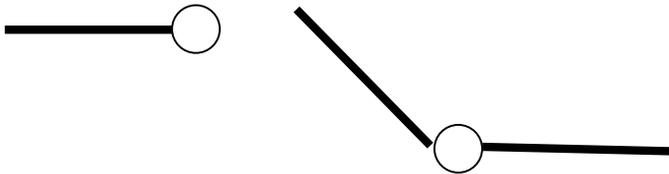


## Circuit Symbols




Wire



Switch (closed  
and open)



Energy source

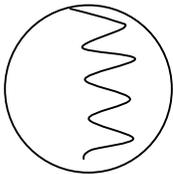

Resistor

## Circuit Diagram

